



DIGITAL LOGIC(H)

Chapter 3 part1: Gate-Level Minimization

2024 Fall

This PowerPoint is for internal use only at Southern University of Science and Technology.
Please do not repost it on other platforms without permission from the instructor.




Today's Agenda

- Recap
- Context
 - Gate level minimization using the Map Method
 - Product of sums simplification
 - Don't Care Conditions
 - Multiple output circuits
- Reading: Textbook, Chapter 3.1-3.5



Recap

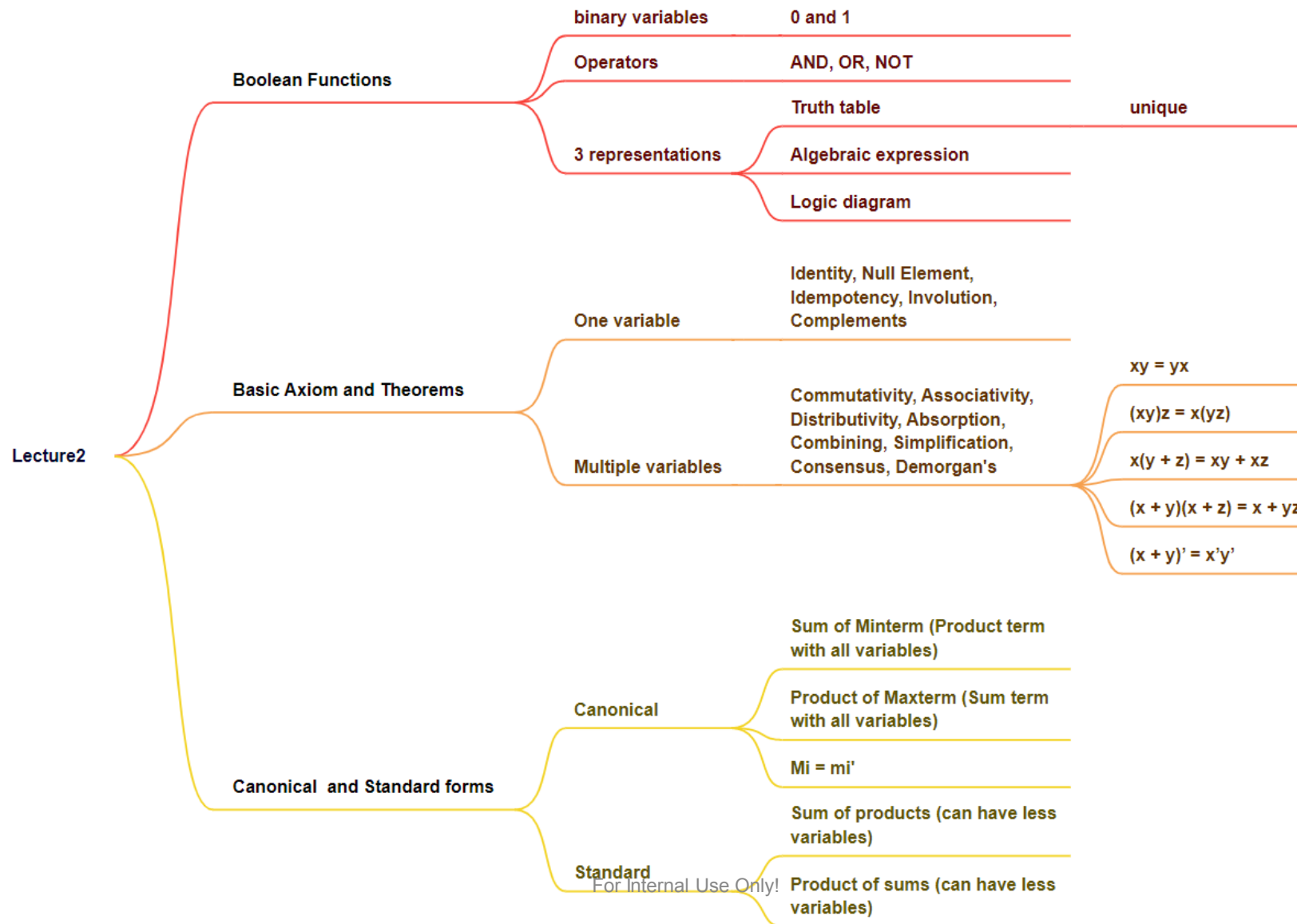

Boolean function simplification

- A function's truth-table representation is unique, while its algebraic expression is not unique.
- Complexity of digital circuit (gate count) \propto complexity of algebraic expression (literal count)
 - $F = x'y'z + x'yz + xy'$ (3 AND term, 8 literals)
 - $F = x'z + xy'$ (2 AND terms, 4 literals)
- The simplest algebraic expression is one that has minimum number of terms with the smallest possible number of literals in each term
- Methods for gate-level minimization:
 - **Algebraic method**(逻辑代数): Boolean algebra (Last lecture)
 - **Karnaugh map**(卡诺图): the map method (This lecture)

Karnaugh Map (K-map)


- An array of squares each representing one minterm to be minimized
- Each K-map defines a unique Boolean function
 - A Boolean function can be represented by a truth table, a Boolean expression, or a map
- K-map is a visual diagram of all possible ways a function may be expressed
- Used for manual minimization of Boolean functions

Merging Minterms

- In function F , m_1 and m_3 in the truth table differ only in one position

001

011

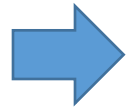



0?1

- ? matches either 0 or 1
- The minterms in a function can be merged to form a simpler product term
 - 001 $\rightarrow x'y'z$
 - 011 $\rightarrow x'yz$
 - 0?1 $\rightarrow x'y'z + x'yz = x'z(y' + y) = x'z$


x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Two-Variable Map

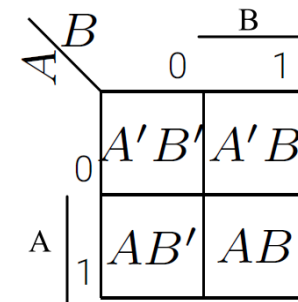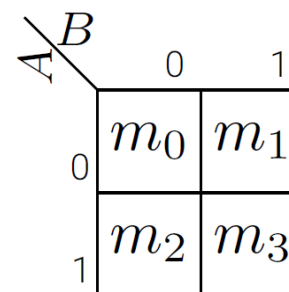- A two-variable map
 - is A truth table in square diagram
 - 4 minterms: $A'B'$, $A'B$, AB' , AB
 - row 0 stands for A' ; row 1 stands for A
 - column 0 stands for B' ; column 1 stands for B



	A	B	F
m_0	0	0	0
m_1	0	1	1
m_2	1	0	1
m_3	1	1	1

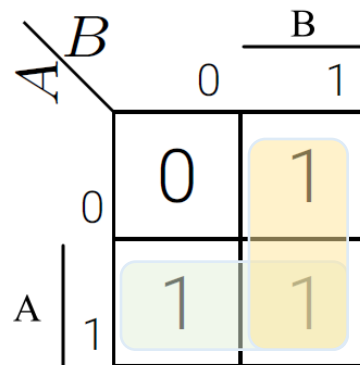

It's ok for groups to overlap, if that makes them larger

$$m_1 + m_2 + m_3 = A'B + AB' + AB = A + B$$



Three-variable Map

- Minterms are arranged in the Gray-code sequence
- Any 2 (horizontally or vertically) adjacent squares differ by exactly 1 variable, which is complemented in one square and uncomplemented in the other.
- Any 2 minterms in adjacent squares that are ORed together will cause a removal of the different variable (adjacent applies not only the middle squares but also the boundary squares)

		B			
		00	01	11	10
A	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6

Three-variable Map

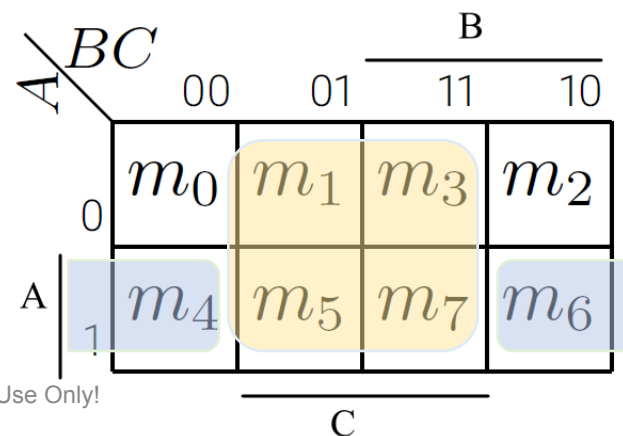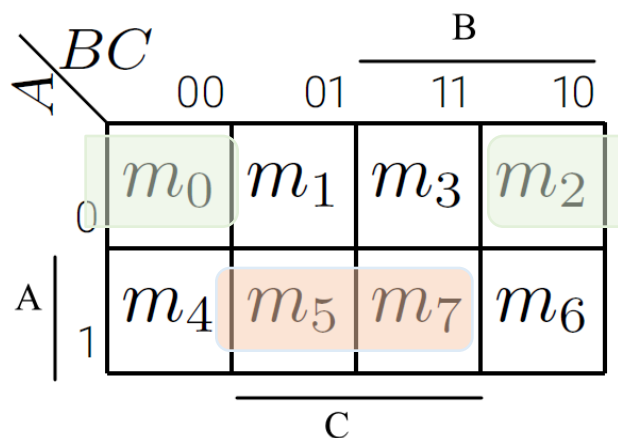- Example (adjacent squares)
- $m_5 + m_7 = AB'C + ABC = AC(B + B') = AC$
- $m_0 + m_2 = A'B'C' + A'BC' = A'C'(B + B') = A'C'$
- $m_4 + m_6 = AB'C' + ABC' = AC'(B' + B) = AC'$
- $m_1 + m_3 + m_5 + m_7$
 $= A'B'C + A'BC + AB'C + ABC = A'C(B + B') + AC(B + B')$
 $= A'C + AC = C$



For Internal Use Only!

Example

- Simplify the following Boolean functions.

$$F = A'BC + A'BC' + AB'C' + AB'C$$

$$= A'B + AB'$$

		B			
		00	01	11	10
A	0	0	0	1	1
	1	1	1	0	0

C

Green circle: $A'BC + A'BC' = A'B$
 Red circle: $AB'C' + AB'C = AB'$

$$F = A'BC + AB'C' + ABC' + ABC$$

$$= BC + AC'$$

		B			
		00	01	11	10
A	0	0	0	1	0
	1	1	0	1	1

C

Green circle: $A'BC + ABC = BC$
 Red circle: $AB'C' + ABC' = AC'$

Example

- Simplify the following Boolean functions.

$$F = \sum(1, 2, 3, 5, 7) = C + A'B$$

		BC			
		00	01	11	10
A	0	0	1	1	1
	1	0	1	1	0

Groups: C (columns 01, 11), $A'B$ (row 0, columns 01, 11, 10)

$$F = \sum(0, 2, 4, 5, 6) = C' + AB'$$

		BC			
		00	01	11	10
A	0	1	0	0	1
	1	1	1	0	1

Groups: C' (columns 00, 01), AB' (row 0, columns 00, 10)

It's ok for groups to overlap,
if that makes them larger

Exercise

- Simplify the following Boolean function.

- $F = A'C + A'B + AB'C + BC$
= ?

$$C + A'B$$

Handwritten Karnaugh map for the function $F = A'C + A'B + AB'C + BC$.

Variables: A (rows), BC (columns).

$A \backslash BC$	00	01	11	10
0	0	1	1	1
1	0	1	1	0

Groupings (circles):

- A circle around the top row (A=0) covers the terms $A'B$ and $A'C$.
- A circle around the middle two columns (BC=01 and BC=11) covers the terms $A'B$ and $AB'C$.

Exercise

- Simplify the following Boolean function.
 - $F = A'C + A'B + AB'C + BC = ?$
- Solution:
 - Express it in sum of minterms.
 - Find the minimal sum of products expression.
 - $F = A'C + A'B + AB'C + BC$

$$= A'C(B+B') + A'B(C+C') + AB'C + (A+A')BC$$

$$= A'BC + A'B'C + A'BC' + A'BC + AB'C + ABC + A'BC$$

$$= \Sigma(1, 2, 3, 5, 7) = C + A'B$$

		B			
		00	01	11	10
A	0	0	1	1	1
	1	0	1	1	0

For Internal Use Only!

Four-Variable Map

- The map
 - 16 minterms
 - Combinations of 2, 4, 8, and 16 adjacent squares

		C			
		00	01	11	10
A	AB \ CD	m_0	m_1	m_3	m_2
	00	m_4	m_5	m_7	m_6
	01	m_{12}	m_{13}	m_{15}	m_{14}
	11	m_8	m_9	m_{11}	m_{10}
	10				
		D			

Implicants

- Implicant: any product term that implies the function

- A product term that makes a function to be true

	minterm	implicant
m_1	✓	✓
m_2	✓	X
$x'z$	X	✓

1-minterm

0-minterm

1 product term

- Prime implicant (PI) (质蕴含)

- A 1-product term obtained by combining the maximum possible number of adjacent squares in the map.

- Essential prime implicant (EPI) (基本质蕴含)

- If a minterm in a square is covered by only one prime implicant



x	y	z	F	
0	0	0	0	m_0
0	0	1	1	m_1
0	1	0	0	m_2
0	1	1	1	m_3
1	0	0	1	m_4
1	0	1	1	m_5
1	1	0	0	m_6
1	1	1	0	m_7

Tips for simplification

- Simplification Steps:
 - Determine all essential prime implicants.
 - Find other prime implicants that cover remaining minterms.
 - Logical sum all prime implicants.
- Tips:
 - Minimize the number of groups
 - Maximize the group size
 - It's ok for groups to overlap, if that makes them larger

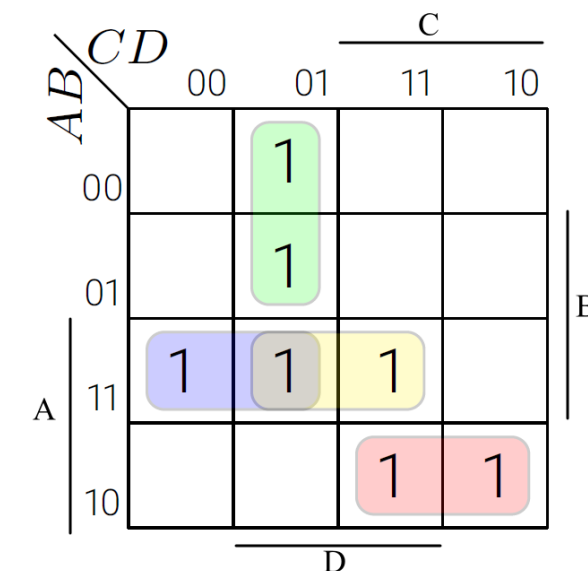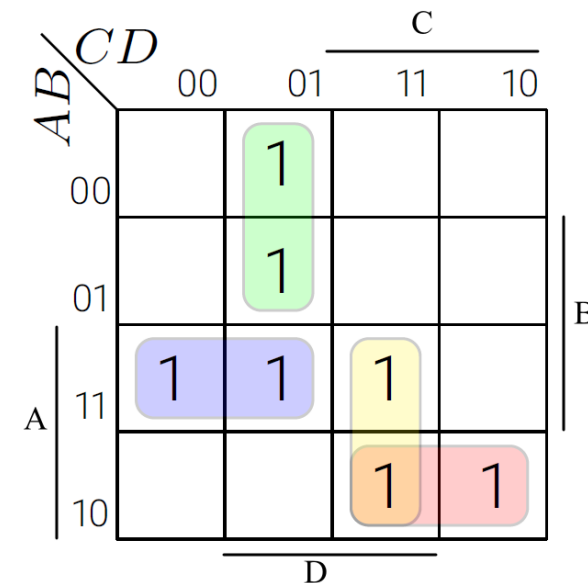Example

- Simplify the following Boolean functions
- $F = m_1 + m_5 + m_{10} + m_{11} + m_{12} + m_{13} + m_{15}$
 - start with EPIs
 - **Green circle:** $A'B'C'D + A'BC'D = A'C'D$
 - **Purple circle:** $ABC'D' + ABC'D = ABC'$
 - **Red circle:** ...
 - ...
- $F = A'C'D + ABC' + \text{ACD} + AB'C$
- This reduced expression is not a unique one
 - If pairs are formed in different ways, the simplified expression will be different.
- $F = A'C'D + ABC' + \text{ABD} + AB'C$




Example

- Simplify the following Boolean functions.

$$F = \sum(7, 9, 10, 11, 12, 13, 14, 15)$$

$$= AB + AC + AD + BCD$$

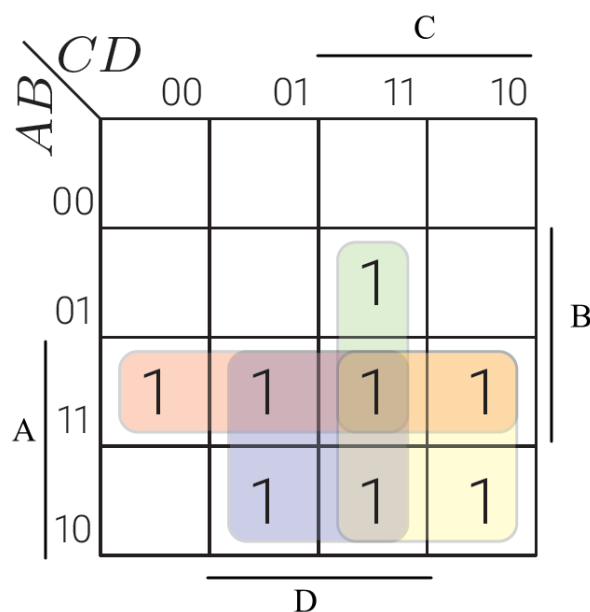

$$F(A,B,C,D) = ABCD + AB'C'D' + AB'C + AB$$


$$= ABCD + AB'C'D' + AB'C(D + D')$$

$$+ AB(C + C')(D + D')$$

$$= \dots$$

$$= \sum(8, 10, 11, 12, 13, 14, 15)$$

$$= AB + AC + AD'$$

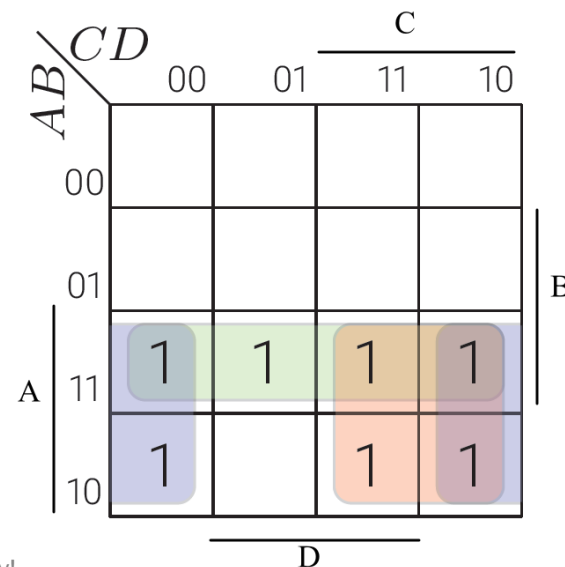

Exercise

- Simplify the following Boolean functions.


$$\begin{aligned} F(A,B,C,D) \\ &= \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14) \\ &= ? \end{aligned}$$

$$\begin{aligned} F(A,B,C,D) \\ &= A'B'C' + B'CD' + A'BCD' + AB'C' \\ &= ? \end{aligned}$$

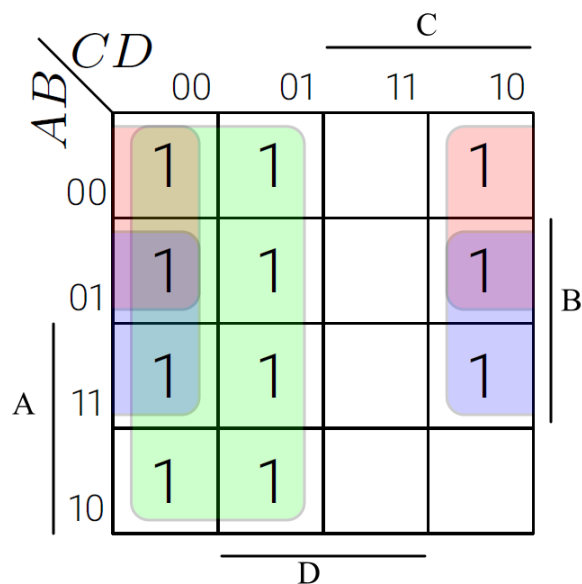
Exercise

- Simplify the following Boolean functions.

$$\begin{aligned}
 F(A,B,C,D) &= \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14) \\
 &= C' + A'D' + BD'
 \end{aligned}$$


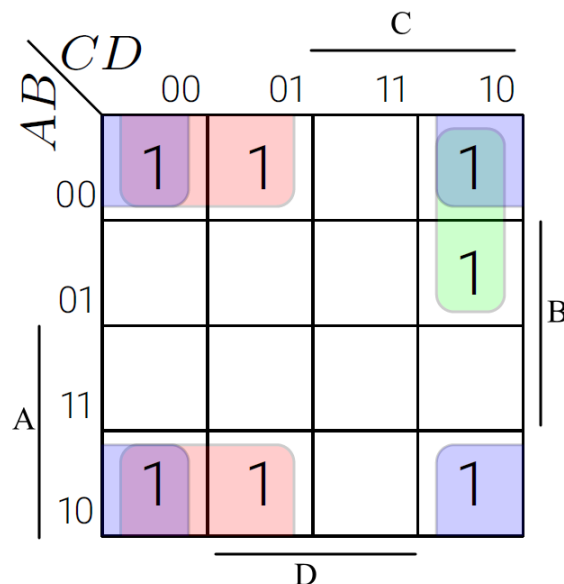
$$\begin{aligned}
 F &= A'B'C' + B'CD' + A'BCD' + AB'C' \\
 &= A'B'C'(D + D') + B'CD'(A + A') + \\
 &\quad A'BCD' + AB'C'(D + D') \\
 &= A'B'C'D + A'B'C'D' + AB'CD' + A'B'CD' + \\
 &\quad A'BCD' + AB'C'D + AB'C'D' \\
 &= \sum(0, 1, 2, 6, 8, 9, 10) \\
 &= B'C' + B'D' + A'CD'
 \end{aligned}$$



K-map Summary

- Any 2^k adjacent squares, $k=0,1,\dots,n$, in an n -variable map represent an area that gives a product term of $n-k$ literals

K	# of adjacent squares	# of literals left in a term in an n-variable map		
		n=2	n=3	n=4
0	1	2	3	4
1	2	1	2	3
2	4	0	1	2
3	8		0	1
4	16			0

- Five-Variable Map
 - Map for more than four variables becomes complicated
 - Five-variable map: two four-variable map (one on the top of the other), contains 2^5 or 32 cells.

Product of Sums Simplification

- Previous Examples are Sum of Product Simplification
 - E.g. $F = AB + A'D + AB'C$ (Product of sum form)
- How to find Product of Sum simplification
 - E.g. $F = (A+B)(B+C')$ (Sum of Product form)
- POS simplification Steps
 - Simplified F' in the form of sum of products
 - Group adjacent 0-minterms squares together
 - Apply DeMorgan's theorem $F = (F')'$
 - F' : sum of products \rightarrow F : product of sums

Example

- Simplify the Boolean function into product of sums form:

- $F(A,B,C,D) = \sum(2, 3, 7, 10, 11, 15)$

- Solution

因为零好圈

- Step1: group the 0-minterms to find **F complement**

$$\begin{aligned} F' &= \sum(0, 1, 4, 5, 6, 8, 9, 12, 13, 14) \\ &= C' + BD' \quad (\text{Group 0 minterms}) \end{aligned}$$

- Step2: find the complement again to get original F

$$\begin{aligned} F &= (F')' = (C' + BD')' \\ &= C(B' + D) \quad (\text{DeMorgan's}) \end{aligned}$$

		C			
		D			
A	AB	00	01	11	10
	00	0	0	1	1
	01	0	0	1	0
	11	0	0	1	0
	10	0	0	1	1

Exercise

- simplify $F(A, B, C, D) = \sum(0, 1, 2, 5, 8, 9, 10)$ into
 - sum-of-products form
 - $F = ?$
 - product-of-sums form
 - $F = ?$

Exercise

- simplify $F(A, B, C, D) = \sum(0, 1, 2, 5, 8, 9, 10)$ into
 - sum-of-products form
 - $F = B'D' + B'C' + A'C'D$ (Group 1-minterms)
 - product-of-sums form
 - $F' = AB + CD + BD'$ (Group 0-minterms)
 - $F = (A'+B')(C'+D')(B'+D)$ (DeMorgan's)

		CD		C	
		00	01	11	10
A	AB	00	01	11	10
	00	1	1	0	1
	01	0	1	0	0
	11	0	0	0	0
	10	1	1	0	1
		D			

B

		CD		C	
		00	01	11	10
A	AB	00	01	11	10
	00	1	1	0	1
	01	0	1	0	0
	11	0	0	0	0
	10	1	1	0	1
		D			

B

Don't care conditions

- Incompletely specified functions
 - Functions that have unspecified outputs for some input combinations
 - E.g. output are unspecified for 1010 to 1111 in 4-bit BCD code
- Don't-care conditions
 - Unspecified minterms of a function, don't-cares, Xs
 - Can be used on a map to provide further simplifications of the Boolean expression
 - Each X can be assigned an arbitrary value, 0 or 1, to help simplification procedure

Example


- Simplify $F(A, B, C, D) = \sum(1, 3, 7, 11, 15)$ with don't-care conditions $d(A, B, C, D) = \sum(0, 2, 5)$.
 - $F = A'B' + CD$
 - or $F = A'D + CD$
 - Just make sure all 1 minterms are circled, thus both simplifications are acceptable

AB \ CD		C			
		00	01	11	10
A	00	X	1	1	X
	01		X	1	
	11			1	
	10			1	
		D			

AB \ CD		C			
		00	01	11	10
A	00	X	1	1	X
	01		X	1	
	11			1	
	10			1	
		D			

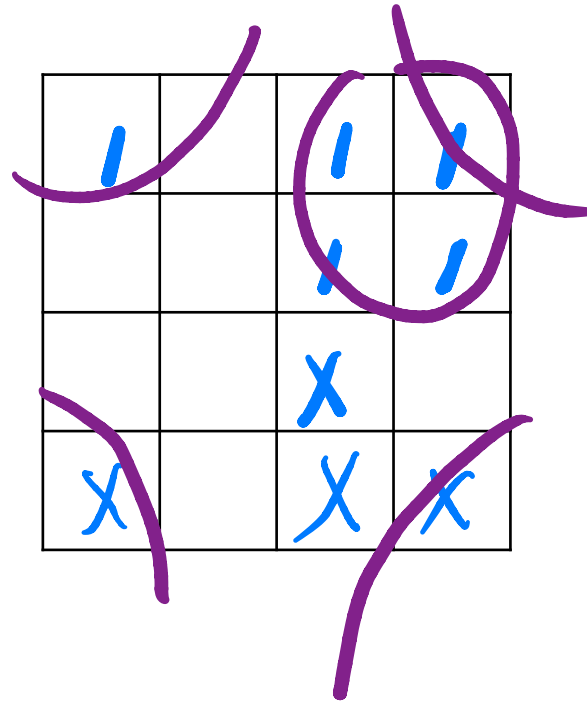Exercise

- Using the Karnaugh map method obtain the minimal sum of the products expression for the function $F(A,B,C,D) = \Sigma(0, 2, 3, 6, 7) + d(8, 10, 11, 15)$




Exercise

- Using the Karnaugh map method obtain the minimal sum of the products expression for the function $F(A,B,C,D) = \Sigma(0, 2, 3, 6, 7) + d(8, 10, 11, 15)$
- $F = A'C + B'D'$


		CD					
		00	01	11	10	C	
A	AB						
	00	1	0	1	1		
	01	0	0	1	1		
	11	0	0	X	0		
	10	X	0	X	X	D	
						B	

Multiple output circuits


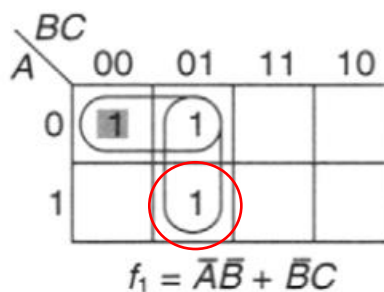
- A circuit with two outputs
 - $f_1 = A'B' + B'C$
 - $f_2 = AC + BC$
 - 6 AND/OR gates in total
- We can optimize the circuit by sharing
 - Find the common term (which might not be the simplest but can be shared)
 - e.g. $AB'C$ (observe the common squares)



(a)

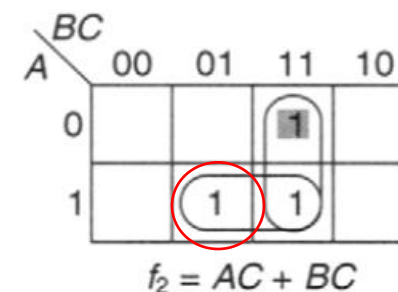

(b)

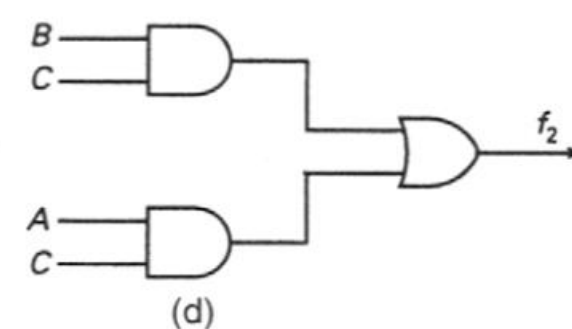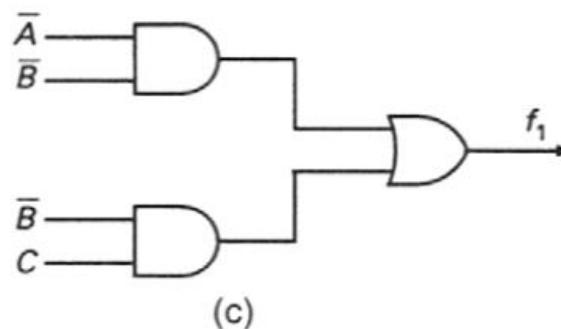

Multiple output circuits

- $AB'C$ is the common minterm
- Thus The circuit can be described as
 - $f_1 = A'B' + AB'C$
 - $f_2 = BC + AB'C$
 - 5 AND/OR gates (less gates)

